

ΑΝΑΦΟΡΑ 3ου set

Κουρκουλος Αγγελος ΑΜ:2017030111

Η άσκηση αυτή ήταν μια επέκταση της προηγούμενης όπου είχε ως σκοπό τη μετατροπή ενός κυκλώματος από λογικές πύλες σε ένα ισοδύναμο κύκλωμα από συνδεδεμένα τρανζίστορ. Ποιό συγκεκριμένα είχαμε ως είσοδο ένα αρχείο όπως αυτό στην άσκηση 2 με τη διαφορά ότι στο netlist του περιέγραφε ένα κυκλωμα από συνδεδεμένες λογικές πύλες και είχε και μια αναφορά προς ένα αρχείο βιβλιοθήκης το οποίο περιείχε την πληροφορία για την μετατροπή κάθε λογικής πύλης που χρειάζεται σε κυκλωμα από τρανζίστορ. Στη συγκεκριμένη βιβλιοθήκη που δημιούργησα με τίτλο MyLib.LIB συμπεριλαμβάνονται οι πύλες NOT , NOR_2 που μας δόθηκαν από την εκφώνηση καθώς και οι NAND_2 και XOR_2 που προσέθεσα με την παρακάτω συνδεσμολογία.

<pre>## GATE NAND_2 ## RAILS VCC 1 ; GND 6 ## INPUTS 2 ; 3 ## OUTPUTS 4 ## NETLIST U1 PMOS 2 1 4 U2 PMOS 3 1 4 U3 NMOS 2 4 5 U4 NMOS 3 5 6 ## END_GATE</pre>	
---	--

```
## GATE XOR_2
```

```
## RAILS
```

```
VCC 1 ; GND 6
```

```
## INPUTS
```

```
2 ; 3
```

```
## OUTPUTS
```

```
5
```

```
## NETLIST
```

```
U1 PMOS 2 1 4
```


```
U2 NMOS 2 4 6
```

```
U3 NMOS 3 4 5
```

```
U4 PMOS 3 5 2
```

```
## END_GATE
```

```
##END LIBRARY
```

 


Τι κύκλωμα που μας ζητήθηκε να δημιουργήσουμε και να προσομοιώσουμε είναι ενός αθρίστη με διάσωση κρατούμενου RCA με 5 bit είσοδου (2 για κάθε full adder και Cin) και 3 bit έξοδου (S0 S1 Cout). Σε κάθε full adder το μέρος AND - OR γίνεται NAND-NAND λόγω De Morgan και η συνδεσμολογία του κυκλώματος καθώς και το αρχείο εισόδου (file2) φαίνονται παρακάτω:

file2:

## LIBRARY	## TEST_VECTORS	## TEST_VECTORS
MyLib.LIB	0 ; 0 ; 0 ; 0 ; 1	1 ; 0 ; 0 ; 0 ; 1
##RAILS	## SIMULATE	## SIMULATE
## INPUTS	## TEST_VECTORS	## TEST_VECTORS
1,2,3,9,10	0 ; 0 ; 0 ; 1 ; 0	1 ; 0 ; 1 ; 0 ; 1
## OUTPUTS	## SIMULATE	## SIMULATE
7,14,15	## TEST_VECTORS	## TEST_VECTORS
## NETLIST	0 ; 0 ; 0 ; 1 ; 1	1 ; 0 ; 1 ; 1 ; 0
G1,XOR_2 ,IN,1,2,OUT,4	## SIMULATE	## SIMULATE
G2,NAND_2,IN,1,2,OUT,5	## TEST_VECTORS	## TEST_VECTORS
G3, XOR_2, IN,3,4, OUT,7	0 ; 0 ; 1 ; 0 ; 0	1 ; 1 ; 1 ; 1 ; 1
G4,NAND_2,IN,3,4,OUT,6	## SIMULATE	## SIMULATE
G5,NAND_2,IN,6,5,OUT,8	## TEST_VECTORS	## END_TEST
G6,XOR_2 ,IN,9,10,OUT,11	0 ; 0 ; 1 ; 0 ; 1	## END_SIMULATION
G7,NAND_2,IN,9,10,OUT,12	## SIMULATE	
G8, XOR_2, IN,8,11, OUT,14	## TEST_VECTORS	
G9,NAND_2,IN,8,11,OUT,13	0 ; 0 ; 1 ; 1 ; 0	
G10,NAND_2,IN,13,12,OUT,15	## SIMULATE	
## TESTBENCH	## TEST_VECTORS	
## TEST_IN	0 ; 0 ; 1 ; 1 ; 1	
10 ; 9 ; 2 ; 1 ; 3	## SIMULATE	
## TEST_OUT	## TEST_VECTORS	
7 ; 14 ; 15	0 ; 1 ; 1 ; 1 ; 1	
## TEST_VECTORS	## SIMULATE	
0 ; 0 ; 0 ; 0 ; 0	## TEST_VECTORS	
## SIMULATE	1 ; 0 ; 0 ; 0 ; 0	
	## SIMULATE	

Όπως βλέπουμε έχουμε πάρει αρκετά δείγματα εισόδων Test_Vectors συμπεριλαμβανομένων όλων των ακραίων περιπτώσεων ώστε να είμαστε σίγουροι για τη λειτουργία του κυκλώματος. Επίσης πρέπει να σημειωθεί ότι οι κόμβοι είσοδου Test_In που βρίσκονται στο αρχείο είναι σε διαφορετική σειρά από ότι είναι οι είσοδοι Inputs έτσι ώστε το test_vector να έχει το Cin και στη συνέχεια το list significant bit με τη σειρά ξεκινώντας από τα δεξιά του.

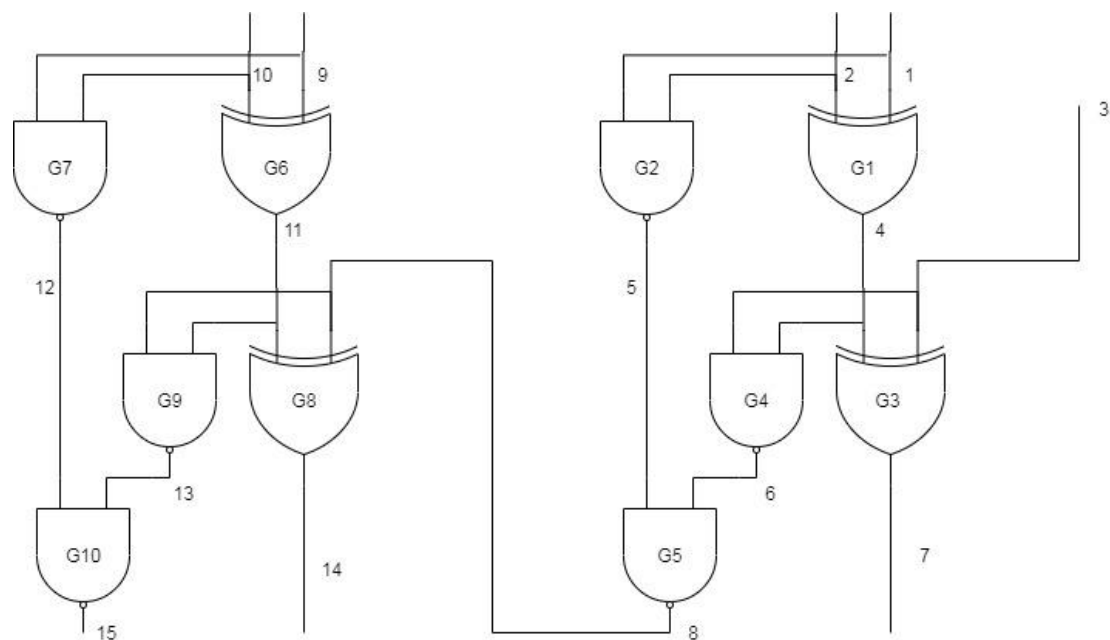Το σχέδιο του κυκλώματος καθώς και οι κόμβοι του φαίνονται παρακάτω:



οι βασικές επεκτάσεις του αλγορίθμου είναι η συνάρτηση initializeLib() που φέρνει στο πρόγραμμα την πληροφορία από τη βιβλιοθήκη και οι συναρτήσεις createFinalNet() και createFinalNetAddMos() οι οποίες συνδυάζουν τις αποθηκευμένες πληροφορίες που έχουν αναγνωστεί από τα αρχεία εισόδου και δημιουργούν ένα τελικό netlist και τις υπόλοιπες απαραίτητες πληροφορίες που χρειάζονται για να περιγράψουν όλο το κύκλωμα σαν συνδεδεμένους κόμβους

Η δομή του αλγορίθμου που υλοποιήθηκε είναι :

```
define the arrays we need to store the information from file
```

```
initialization(...)
```

```
//it stores the information from file in the appropriate array
```

define the arrays we need to store the information from Library

```
initializeLib(...)          //it stores the information from Library in the appropriate array
```

define the arrays we need to store the converted information we will create from Library and file arrays

```
while(flag==1){ /// loop we need in case that the gates are not with the correct order in the starting netlist
```

```
    flag=0;
```

```
    int c=0;
```

```
    while(netlist[c]!= 0){ ///Loop for every gate
```

```
        if(logicgate[c]==NOT){ /// for every case of Lgate call the func createFinalNet to add the gate to final
            createFinalNet(...);                                     /// netlist
```

```
        }
```

```
        else if(logicgate[c]==NOR_2){
```

```
            createFinalNet(...)
```

```
        }
```

```
        else if(logicgate[c]==NAND_2){
```

```
            createFinalNet(...)
```

```
        }
```

```
        else if(logicgate[c]==XOR_2){
```

```
            createFinalNet(...)
```

```
        }
```

```
        else if(logicgate[c]==NMOS || PMOS){ ///add the transistor to final netlist
```

```
            createFinalNetAddMos(...)
```

```
        }
```

```
    }
```

```
}
```

```
while (testvector[i] != 0){ //Loop for every testVector
```

```
    while(check==1){ //Loop that run until nothing changed so we done
```

```
        check=0;
```

```
        j=0;
```

```
        while(transistor[j]!=0){ // Loop for every transistor
```

```
            if(transistor[j]==PMOS && newNode[netlist[j]][0]==0 ){
```

```
                ...
```

```
                check=1;
```

```
            }
```

```
            else if(transistor[j]==PMOS && newNode[netlist[j]][0]==1 ){
```

```
                ...
```

```
                check=1;
```

```
            }
```

```
            else if(transistor[j]==NMOS && newNode[netlist[j]][0]==0 ){
```

```
                ...
```

```
                check=1;
```

```
            }
```

```
            else if(transistor[j]==NMOS && newNode[netlist[j]][0]==1 ){
```

```
                ...
```

```
                check=1;
```

```
            }
```

```
        }
```

```

    }
    i++;
}

```

Τα αποτελέσματα του αλγορίθμου για το αρχείο εισόδου που υπάρχει παραπάνω είναι:

```

For the 0 TEST_VECTORS the output 7 is : 0
the output 14 is : 0
the output 15 is : 0
For the 1 TEST_VECTORS the output 7 is : 1
the output 14 is : 0
the output 15 is : 0
For the 2 TEST_VECTORS the output 7 is : 1
the output 14 is : 0
the output 15 is : 0
For the 3 TEST_VECTORS the output 7 is : 0
the output 14 is : 1
the output 15 is : 0
For the 4 TEST_VECTORS the output 7 is : 1
the output 14 is : 0
the output 15 is : 0
For the 5 TEST_VECTORS the output 7 is : 0
the output 14 is : 1
the output 15 is : 0
For the 6 TEST_VECTORS the output 7 is : 0
the output 14 is : 1
the output 15 is : 0
For the 7 TEST_VECTORS the output 7 is : 1
the output 14 is : 1
the output 15 is : 0
For the 8 TEST_VECTORS the output 7 is : 1
the output 14 is : 0
the output 15 is : 1
For the 9 TEST_VECTORS the output 7 is : 0
the output 14 is : 1
the output 15 is : 0
For the 10 TEST_VECTORS the output 7 is : 1
the output 14 is : 1
the output 15 is : 0
For the 11 TEST_VECTORS the output 7 is : 0
the output 14 is : 0
the output 15 is : 1
For the 12 TEST_VECTORS the output 7 is : 0
the output 14 is : 0
the output 15 is : 1
For the 13 TEST_VECTORS the output 7 is : 1
the output 14 is : 1
the output 15 is : 1

```

Μπορούμε να δούμε ότι για τις άκρες περιπτώσεις:

Test_Vector0: 0 ; 0 ; 0 ; 0 ; 0 = B1;B0;A1;A0;Cin

Result : out 15 ; out 14 ; out 7 = 0 ; 0 ; 0 = Cout ; S1 ; S0

Test_Vector13: 1 ; 1 ; 1 ; 1 ; 1 = B1;B0;A1;A0;Cin

Result : out 15 ; out 14 ; out 7 = 1 ; 1 ; 1 = Cout ; S1 ; S0

Ενώ για μια μέση περίπτωση π.χ. :

Test_Vector7: 0 ; 0 ; 1 ; 1 ; 1 = B1;B0;A1;A0;Cin


```
For the 0 TEST_VECTORS the output 7 is : 0
the output 14 is : 1
```

```


the output 15 is : 1
Node 5 of gate NAND_2 number 3 is short-circuited
Node 5 of gate NAND_2 number 6 is short-circuited
For the 1 TEST_VECTORS the output 7 is : 1
the output 14 is : 1
the output 15 is : 1
Node 5 of gate NAND_2 number 3 is short-circuited
Node 5 of gate NAND_2 number 6 is short-circuited
For the 2 TEST_VECTORS the output 7 is : 1
the output 14 is : 2
the output 15 is : 1
Node 5 of gate NAND_2 number 6 is short-circuited
For the 3 TEST_VECTORS the output 7 is : 0
the output 14 is : 1
the output 15 is : 1
Node 5 of gate NAND_2 number 2 is short-circuited
Node 5 of gate NAND_2 number 3 is short-circuited
Node 5 of gate NAND_2 number 6 is short-circuited
For the 4 TEST_VECTORS the output 7 is : 1
the output 14 is : 2
the output 15 is : 1
Node 5 of gate NAND_2 number 6 is short-circuited
For the 5 TEST_VECTORS the output 7 is : 0
the output 14 is : 1
the output 15 is : 1
Node 5 of gate NAND_2 number 2 is short-circuited
Node 5 of gate NAND_2 number 6 is short-circuited
For the 6 TEST_VECTORS the output 7 is : 0
the output 14 is : 1
the output 15 is : 1
Node 5 of gate NAND_2 number 1 is short-circuited
Node 5 of gate NAND_2 number 3 is short-circuited
Node 5 of gate NAND_2 number 6 is short-circuited
For the 7 TEST_VECTORS the output 7 is : 1
the output 14 is : 1
the output 15 is : 1
Node 5 of gate NAND_2 number 1 is short-circuited
Node 5 of gate NAND_2 number 3 is short-circuited
Node 5 of gate NAND_2 number 6 is short-circuited
For the 8 TEST_VECTORS the output 7 is : 1
the output 14 is : 0
the output 15 is : 1
Node 5 of gate NAND_2 number 1 is short-circuited
Node 5 of gate NAND_2 number 3 is short-circuited
Node 5 of gate NAND_2 number 5 is short-circuited
Node 5 of gate NAND_2 number 6 is short-circuited

```

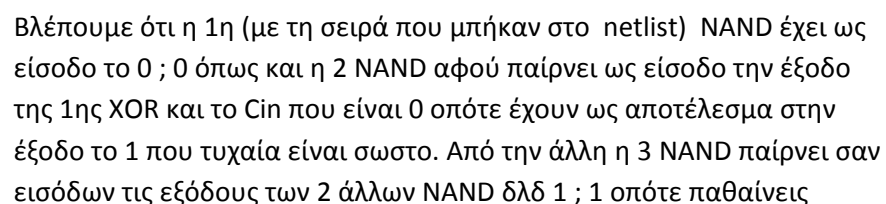Βρίσκει το πρόγραμμα τα βραχικυκλοματα σε σωστά σημεία? Ας πάρουμε σαν παράδειγμα την πρώτη περίπτωση όπου έχουμε `test_vector=0 ; 0 ; 0 ; 0 ; 0`



 βραχυκύκλωμα στον κόμβο 5 το οποίο είναι ένα από τα βραχικικλοματα που βρίσκει ο αλγοριθμος.



Βραχικικλοματα για το παραπάνω παράδειγμα .

Σημείωση: το file1 που υπάρχει στο παραδοτέο είναι το κύκλωμα and από μια NOR και 2 NOT που μας δίνεται από την εκφώνηση